



ECE 362


Microprocessor Systems and Interfacing
Single Cycle Processor

Spring 2025

Reading

- P&H textbook chapter 4.1-4.4: The Single Cycle Processor

Processor Implementation

 


Outline

- Datapath - single cycle
 - single instruction
- Control


Datapath for Instructions

- Single-cycle datapath
- Compose using well-understood pieces
 - Mux, flip-flops and gates
 - ALU
 - Register file


Comb. Logic Elements

 

Adder

 


ALU

 


Mux


Storage Elements

 

- Register
 - for PC

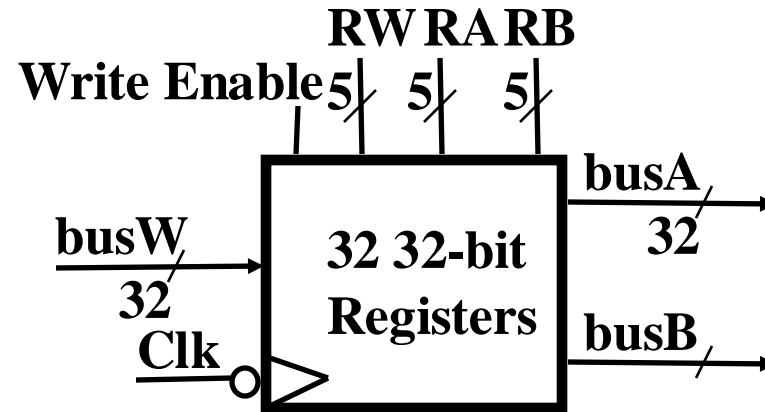


 - Register file
 - 32 registers
 - 2 read ports/buses
 - 1 write port/bus



- Memory
 - 1 input bus
 - 1 output bus
 - Not bidirectional


Computer as State Machine

 


- Storage elements
 - Memory, Register file, PC
- Combinational elements
 - ALUs, Adders, Muxes

Processor Implementation

- This Lecture: Datapath

 

Processor Implementation

 


- Implementation determines
 - How many Clocks Per Instruction (CPI)
 - How long is the clock cycle (Cycle time)
- ISA, compiler determine
 - How many instructions in a program (Instr. count)
- 362 is focused on functionality only
 - Performance is the primary topic of 437

Datapath – Single cycle

- Assumption: Get one whole instruction done in one long clock cycle
 - **fetch, decode/read operands, execute, memory, writeback**
 - 5 steps you should NEVER forget!
 - useful way to represent steps and identify required datapath elements:
RTL
- For single instruction
- Put it together

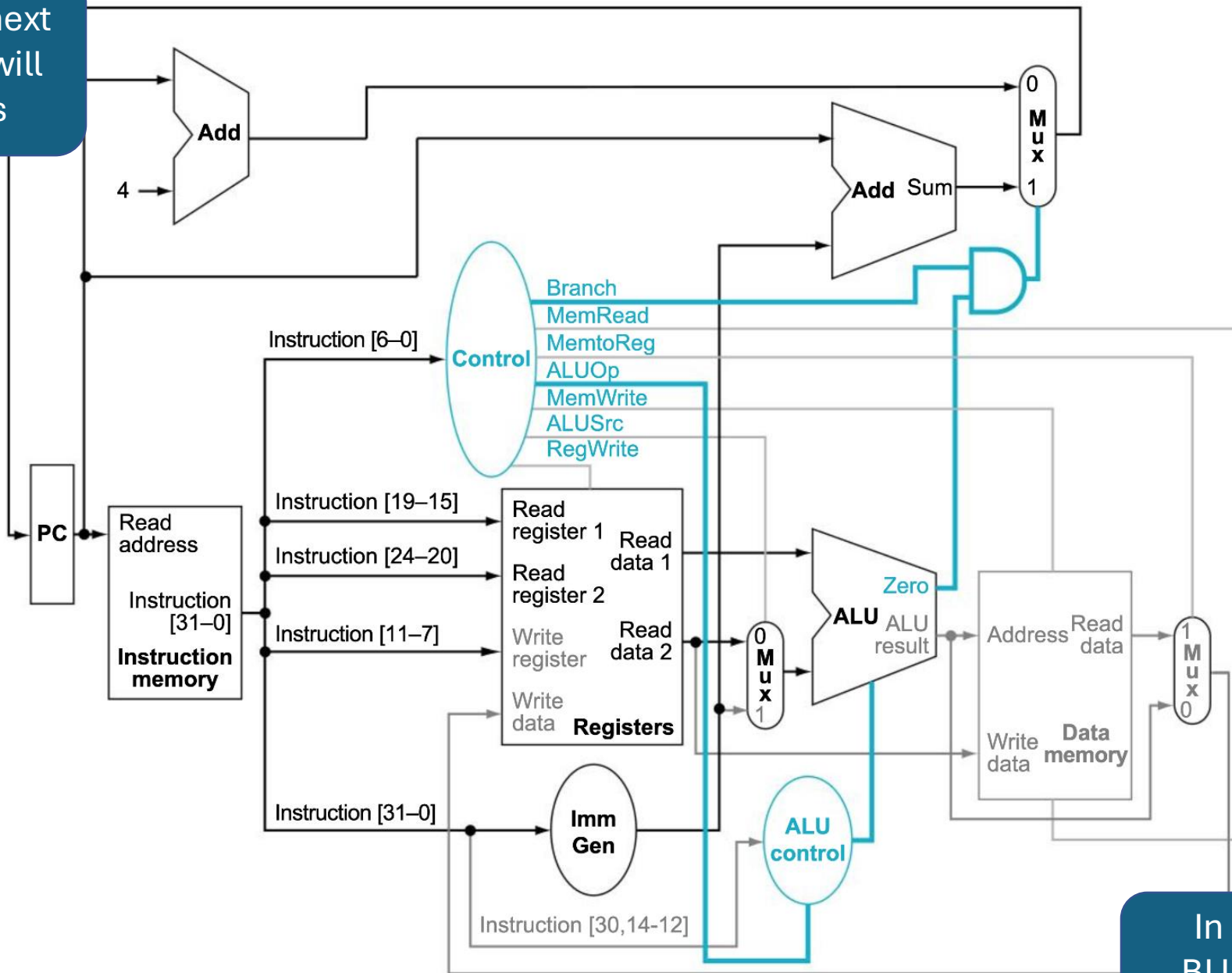By the end of the next few lectures you will understand this



In 437 you will BUILD this! And much, much more.

A Simple Implementation

- add and sub
 - add rd, rs1, rs2
 - addi rd, rs1, imm12
 - sub rd, rs1, rs2
- lw/sw
 - lw rd, imm12(rs1)
 - sw rs2, imm12(rs1)
- branch:
 - beq rs1, rs2, imm12
- Logical ops:
 - and rd, rs1, rs2
 - andi rd, rs1, imm12
 - or rd, rs1, rs2
 - ori rs, rs1, imm12

| Name (Bit position) | Fields | | | | | |
|------------------------|-----------------|-------|-------|--------|---------------|--------|
| | 31:25 | 24:20 | 19:15 | 14:12 | 11:7 | 6:0 |
| (a) R-type | funct7 | rs2 | rs1 | funct3 | rd | opcode |
| (b) I-type | immediate[11:0] | | rs1 | funct3 | rd | opcode |
| (c) S-type | immed[11:5] | rs2 | rs1 | funct3 | immed[4:0] | opcode |
| (d) SB-type | immed[12,10:5] | rs2 | rs1 | funct3 | immed[4:1,11] | opcode |

Register Transfer Language

- RTL gives the meaning of the instructions
- All start by fetching the instruction

fun7 | rs2 | rs1 | fun3 | rd | op = **MEM[PC] // r-type**

imm12 | rs1 | fun3 | rd | op = **MEM[PC] // i-type**

imm7 | rs2 | rs1 | fun3 | imm5 | op = MEM[PC] // s-type/sb-type

inst **Register Transfers**

ADD **R[rd] ← R[rs1] + R[rs2];** **PC ← PC + 4**

SUB **R[rd] ← R[rs1] – R[rs2];** **PC ← PC + 4**


```
LOAD    R[rd] <- MEM[ R[rs1] + sign_ext(imm12)];  PC <- PC + 4
```

```
STORE    MEM[ R[rs1] + sign_ext(imm7 || imm5) ] <- R[rs2]; PC <- PC + 4
```

```
BEQ      if ( R[rs1] == R[rs2] ) then PC <- PC + sign_ext(imm7 || imm5)* || 0
          else PC <- PC + 4
```

Fetch Instructions

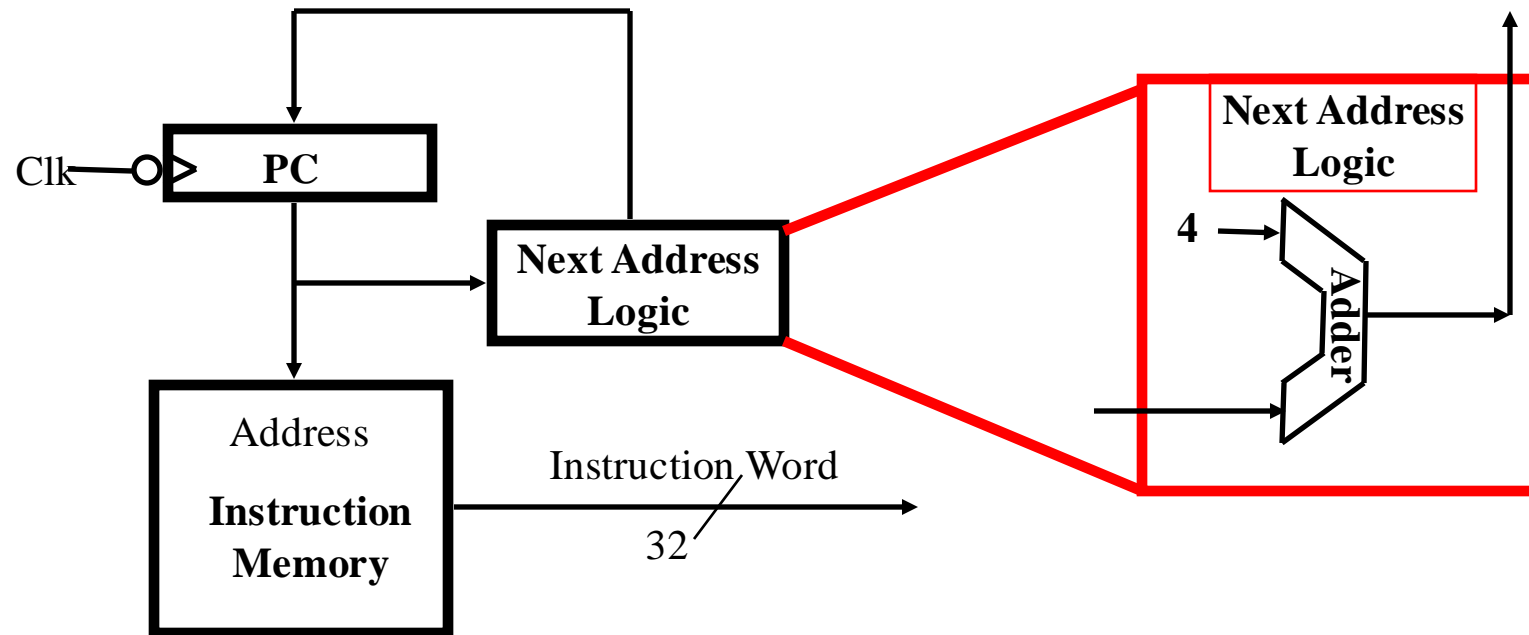
- Fetch instruction, then update PC
- PC updated (at the end of) every cycle
 - What if no branches or jumps?



ALU Instructions


- $R[rd] \leftarrow R[rs1] \text{ op } R[rs2]$ Example: `add rd, rs1, rs2`
 - Ra, Rb, and Rw come from instruction's rs1, rs2, and rd fields
 - ALUOperation and RegWr: control logic after decoding the instruction

| Name (Bit position) | Fields | | | | | |
|------------------------|--------|-------|-------|--------|------|--------|
| | 31:25 | 24:20 | 19:15 | 14:12 | 11:7 | 6:0 |
| (a) R-type | funct7 | rs2 | rs1 | funct3 | rd | opcode |

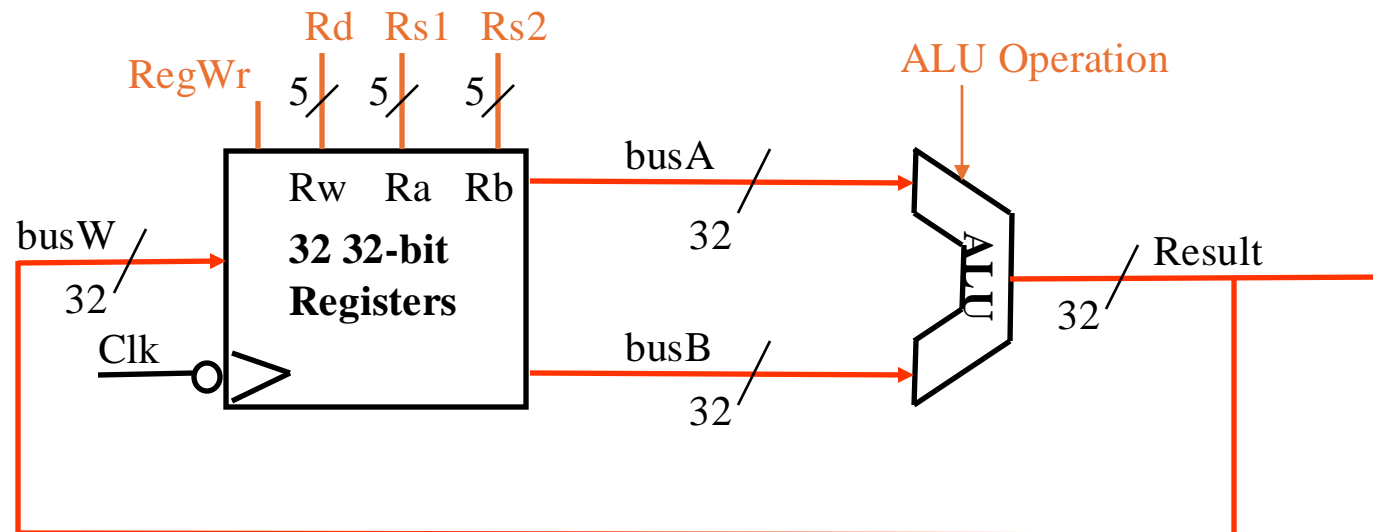


Load Instruction

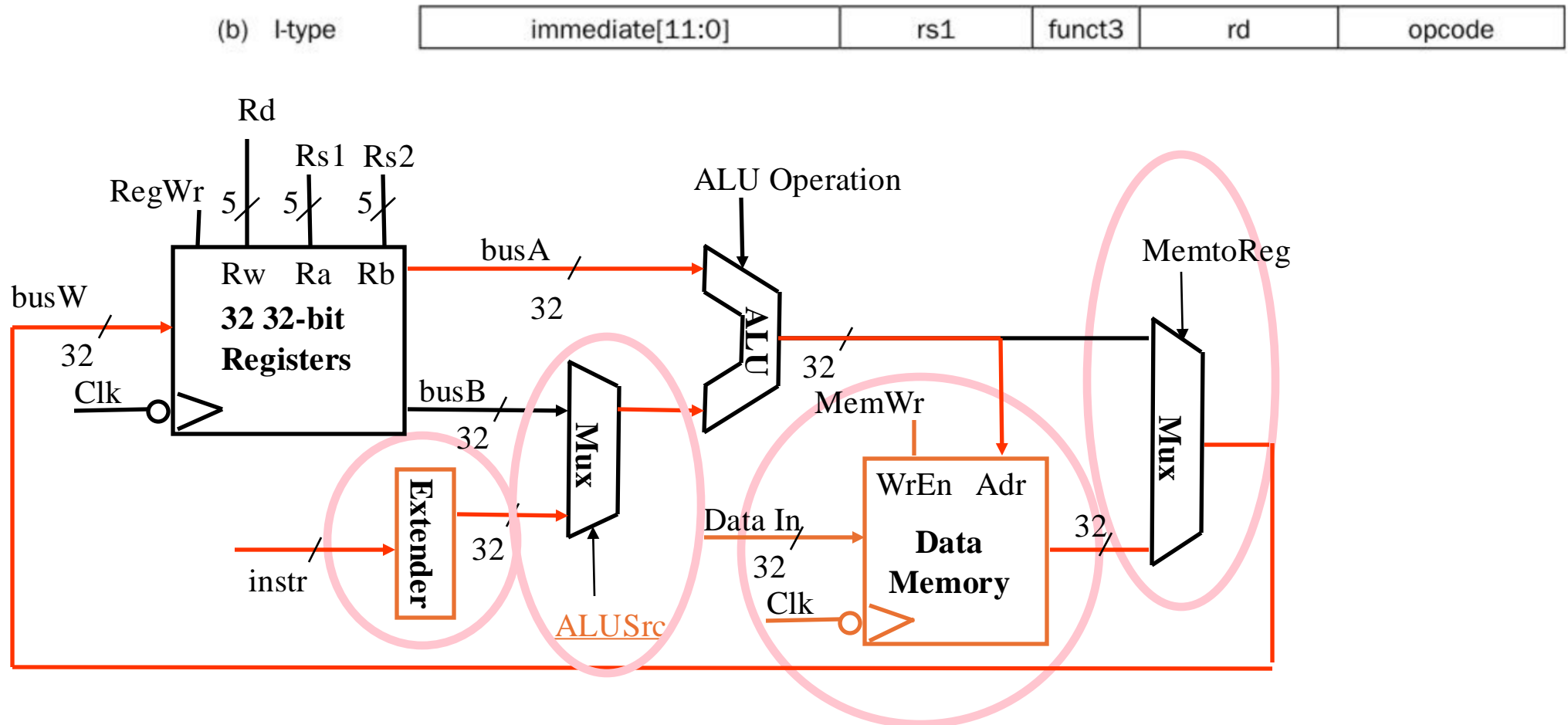- $R[\text{rd}] \leftarrow \text{Mem}[R[\text{rs1}] + \text{SignExt}[\text{imm12}]]$
- Example: `lw rd, imm12(rs1)`



Store Instruction

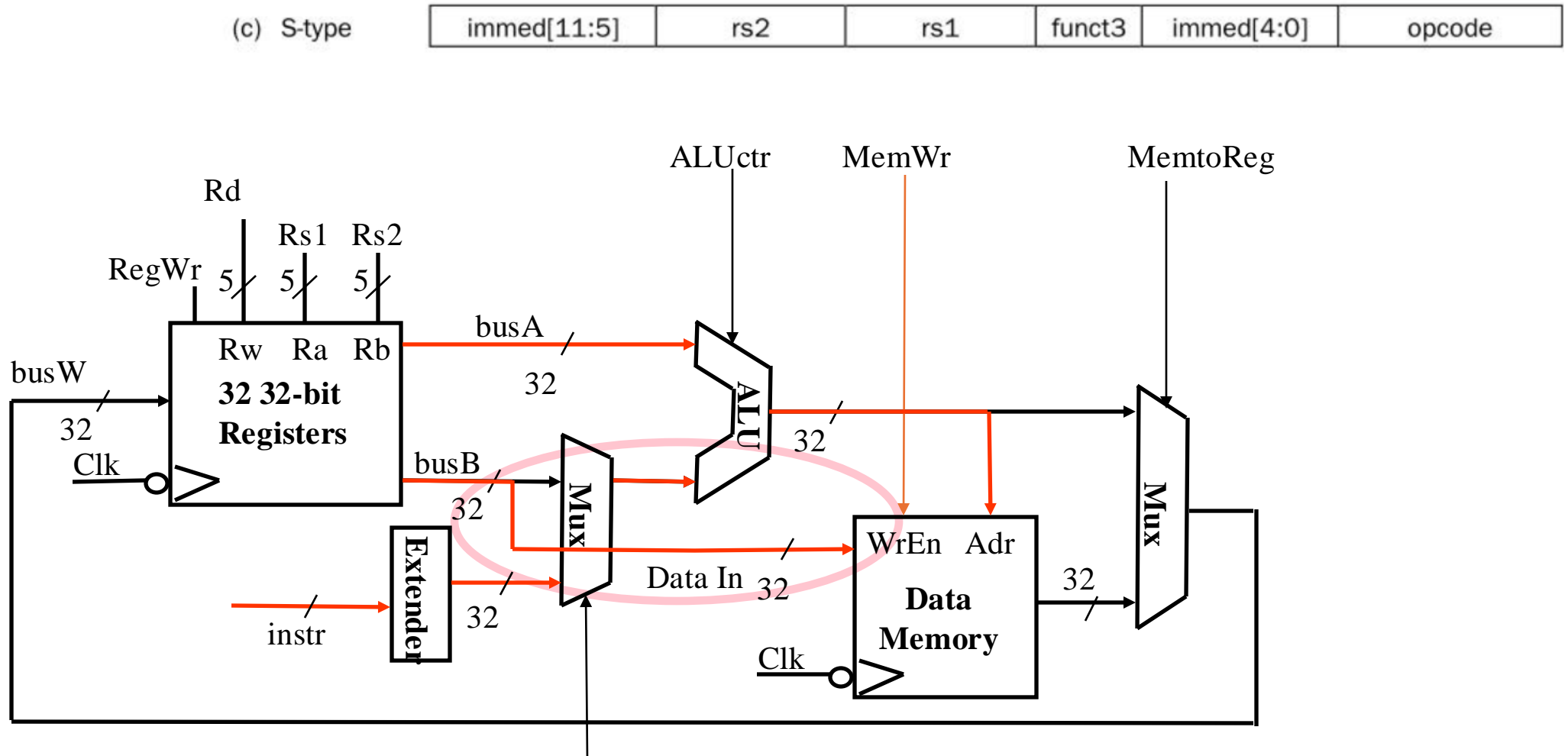- $\text{Mem}[R[\text{rs1}] + \text{SignExt}[\text{imm11:5} \parallel \text{imm4:0}]] \leftarrow R[\text{rs2}]$ Example: `sw rs2, imm12(rs1)`



Conditional Branch Instruction





- beq rs1, rs2, imm12
 - $IR = Mem[PC]$ // Fetch the instruction from memory
 - if ($R[rs1] == R[rs2]$) // Calculate the next instruction's address
 - $PC \leftarrow PC + (SignExt(imm12) \ll 1)$
 - else
 - $PC \leftarrow PC + 4$
- Branches compute TWO things: branch condition and branch target


Datapath for 'beq'

- beq rs1, rs2, imm12
 - Datapath generates branch condition (zero)

(d) SB-type

| | | | | | |
|----------------|-----|-----|--------|---------------|--------|
| immed[12,10:5] | rs2 | rs1 | funct3 | immed[4:1,11] | opcode |
|----------------|-----|-----|--------|---------------|--------|

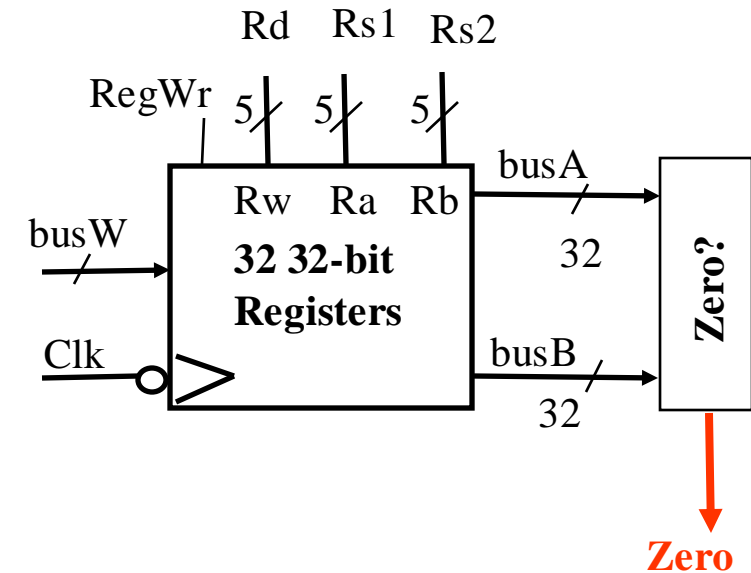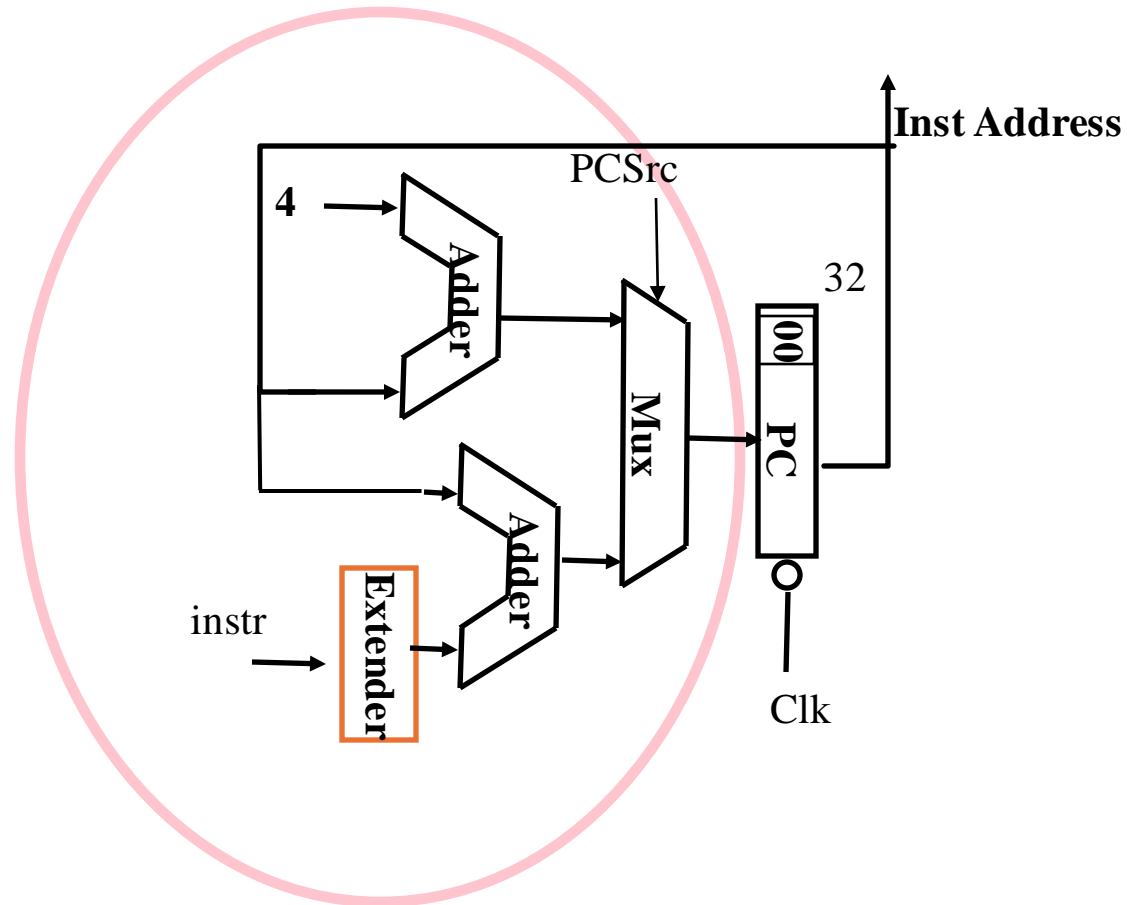

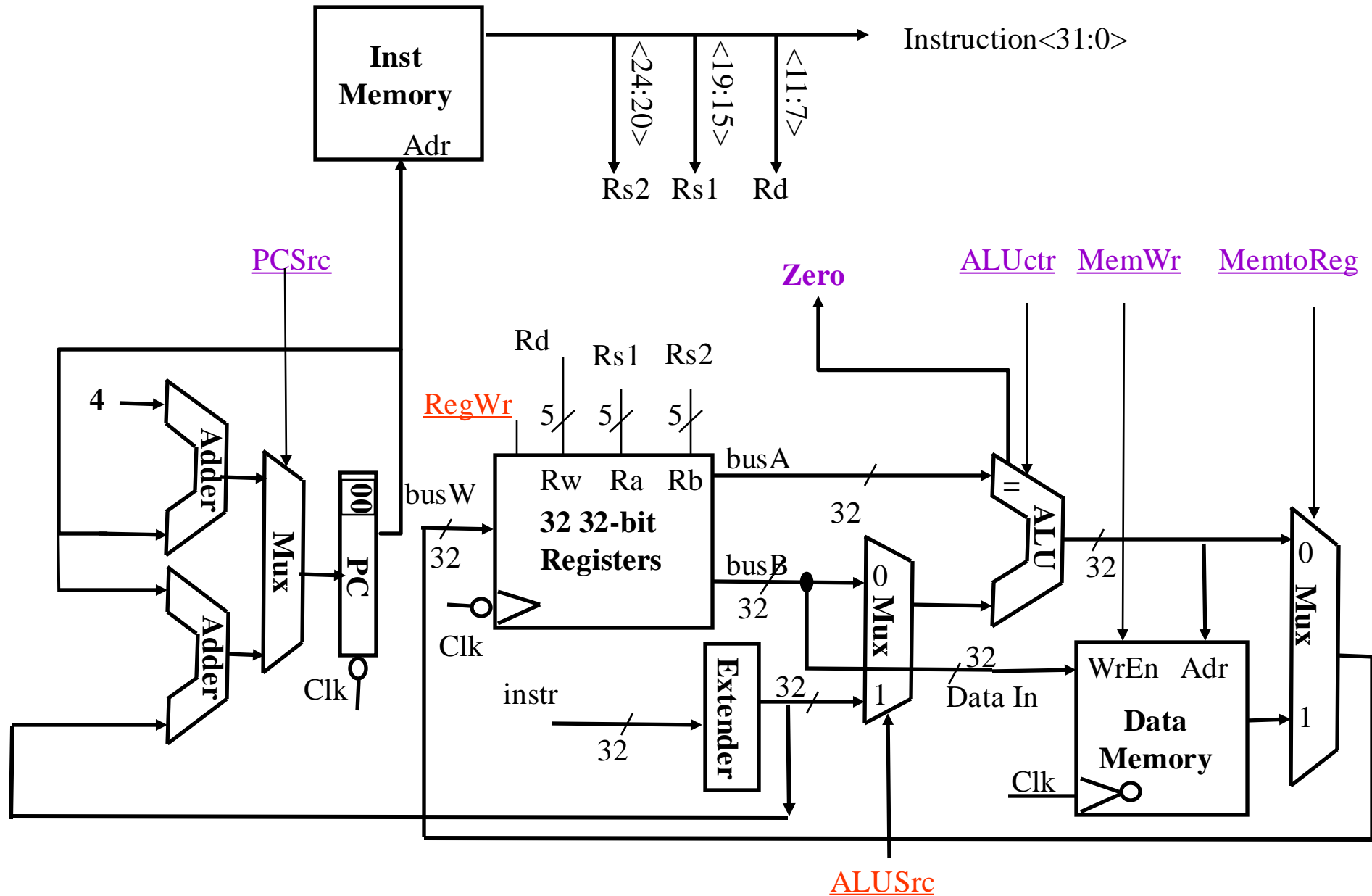


Summary

- For a given instruction
 - Describe operation in RTL
 - Use ALUs, Registers, Memory, adders to achieve required functionality
- To add instructions
 - Rinse and repeat; Reuse components via muxes
 - Not all blocks are used by all instructions so you need to ensure unused blocks don't interfere
- Control: next
 - Selection controls for muxes
 - ALU controls for ALU ops
 - Register address controls
 - Write enables for registers/memory


Exercise

- See worksheet
- Highlight active datapath for
 - add
 - beq
 - sw
 - lw


add

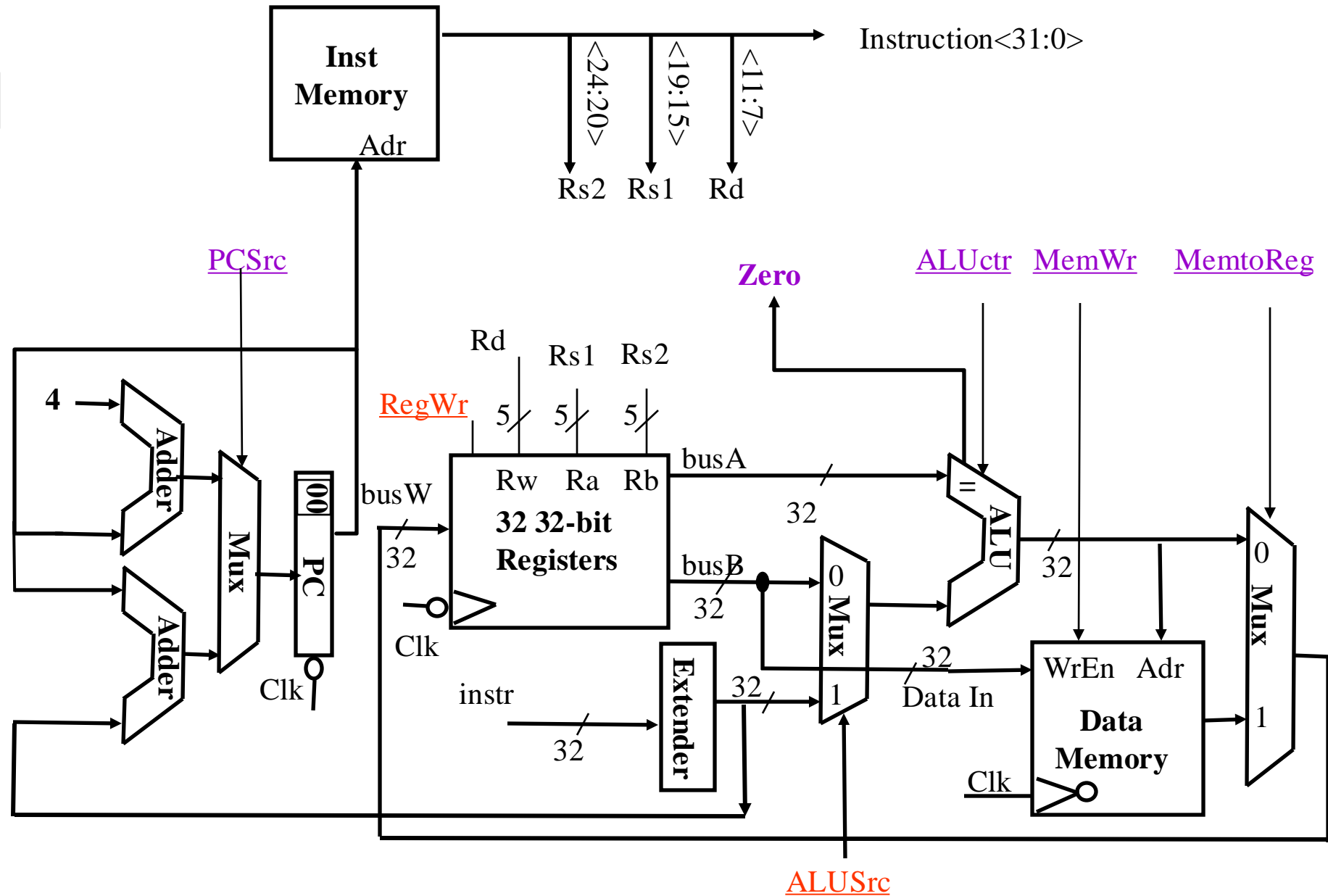


beq

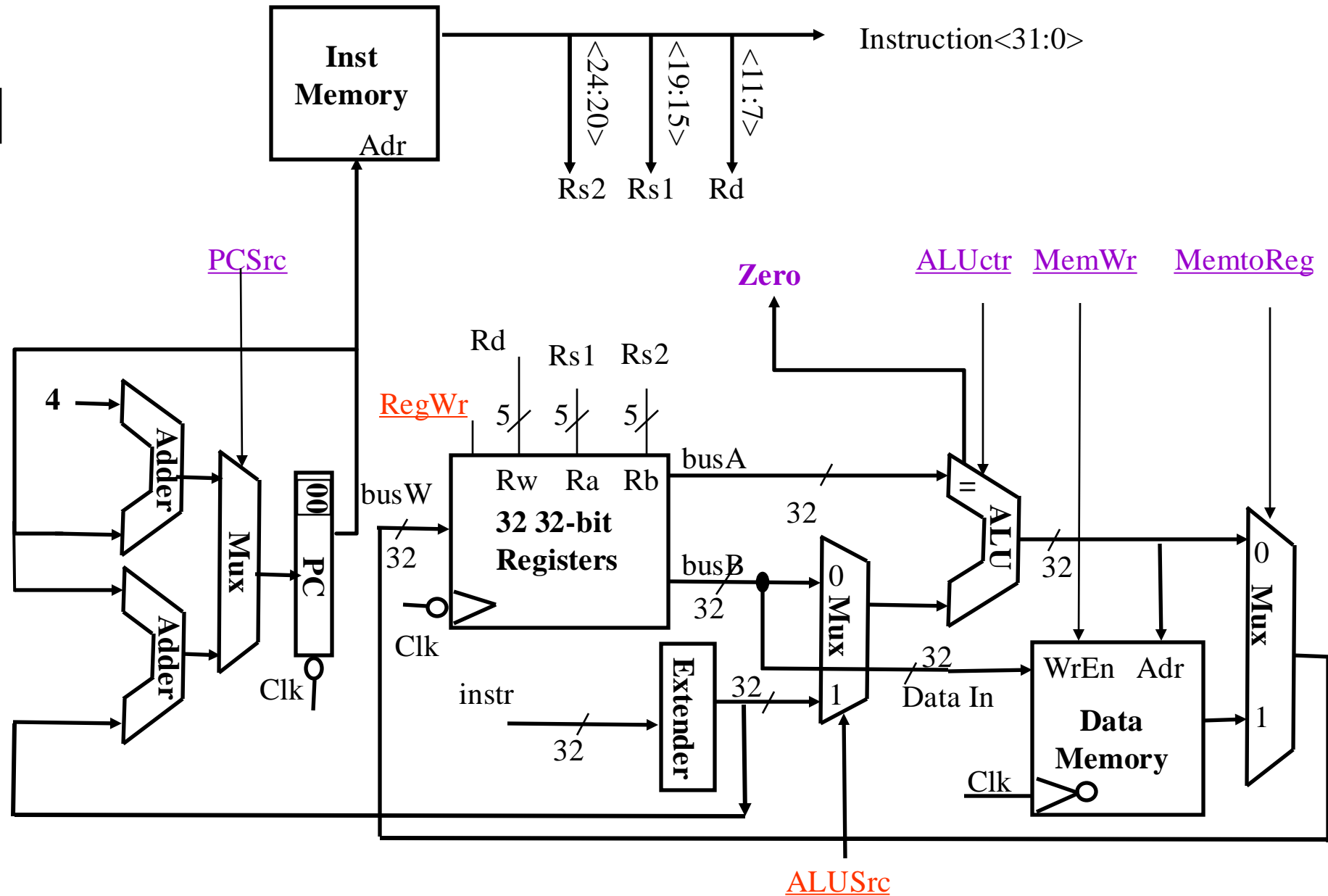

SW

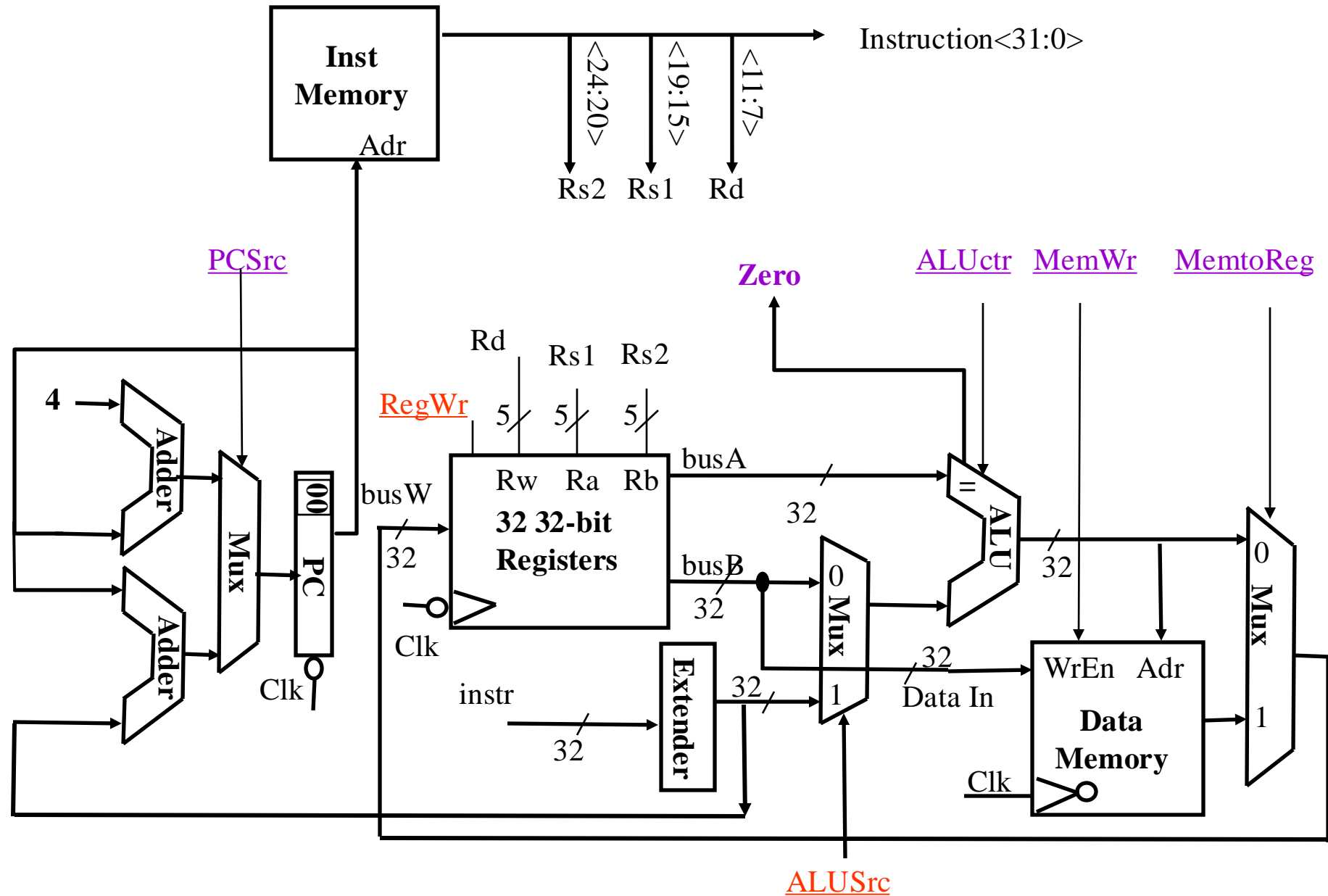


lw

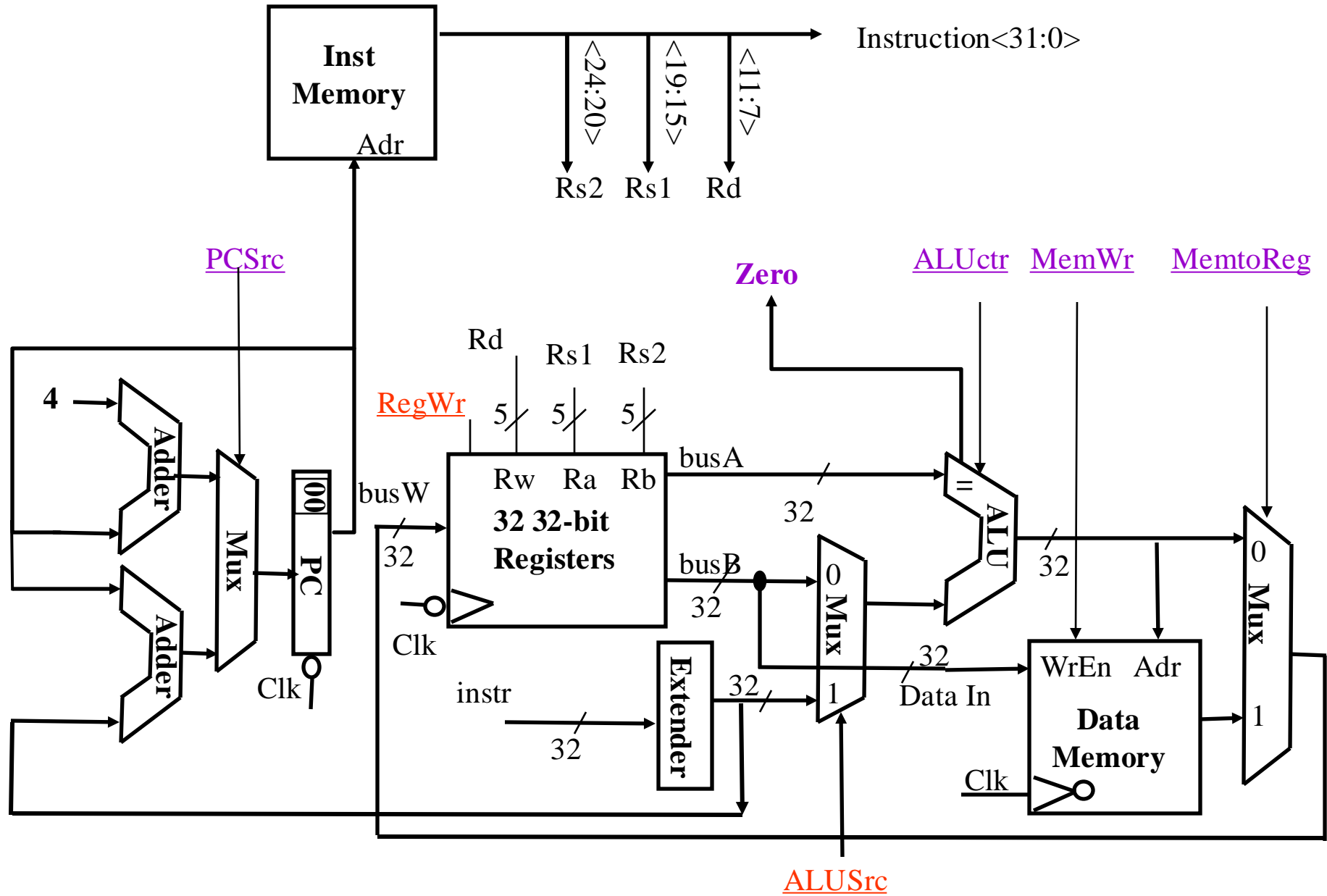


Processor Implementation

- This Lecture: Control

 


Control for Datapath

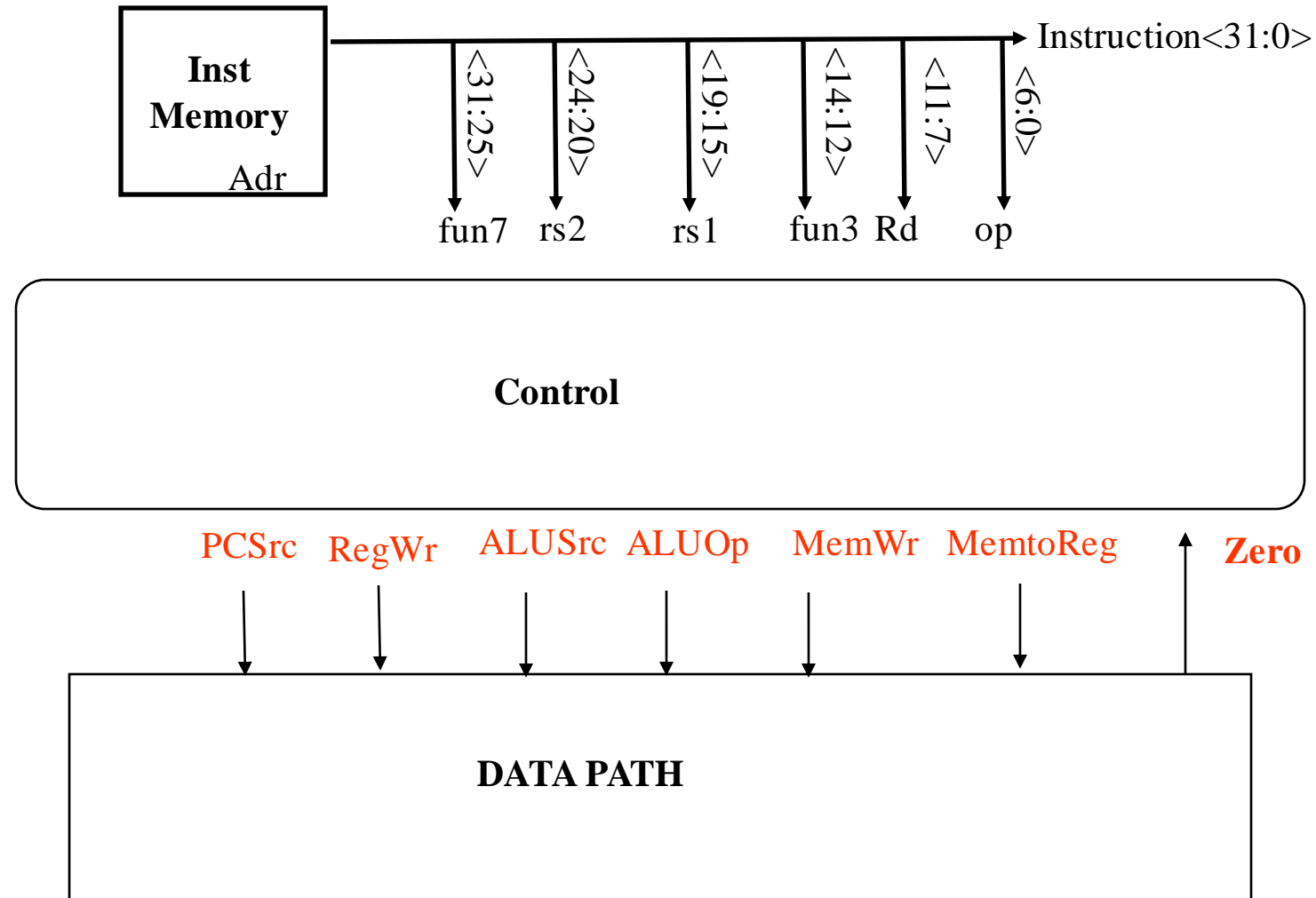


Controls for Add Operation

- $R[rd] = R[rs1] + R[rs2]$

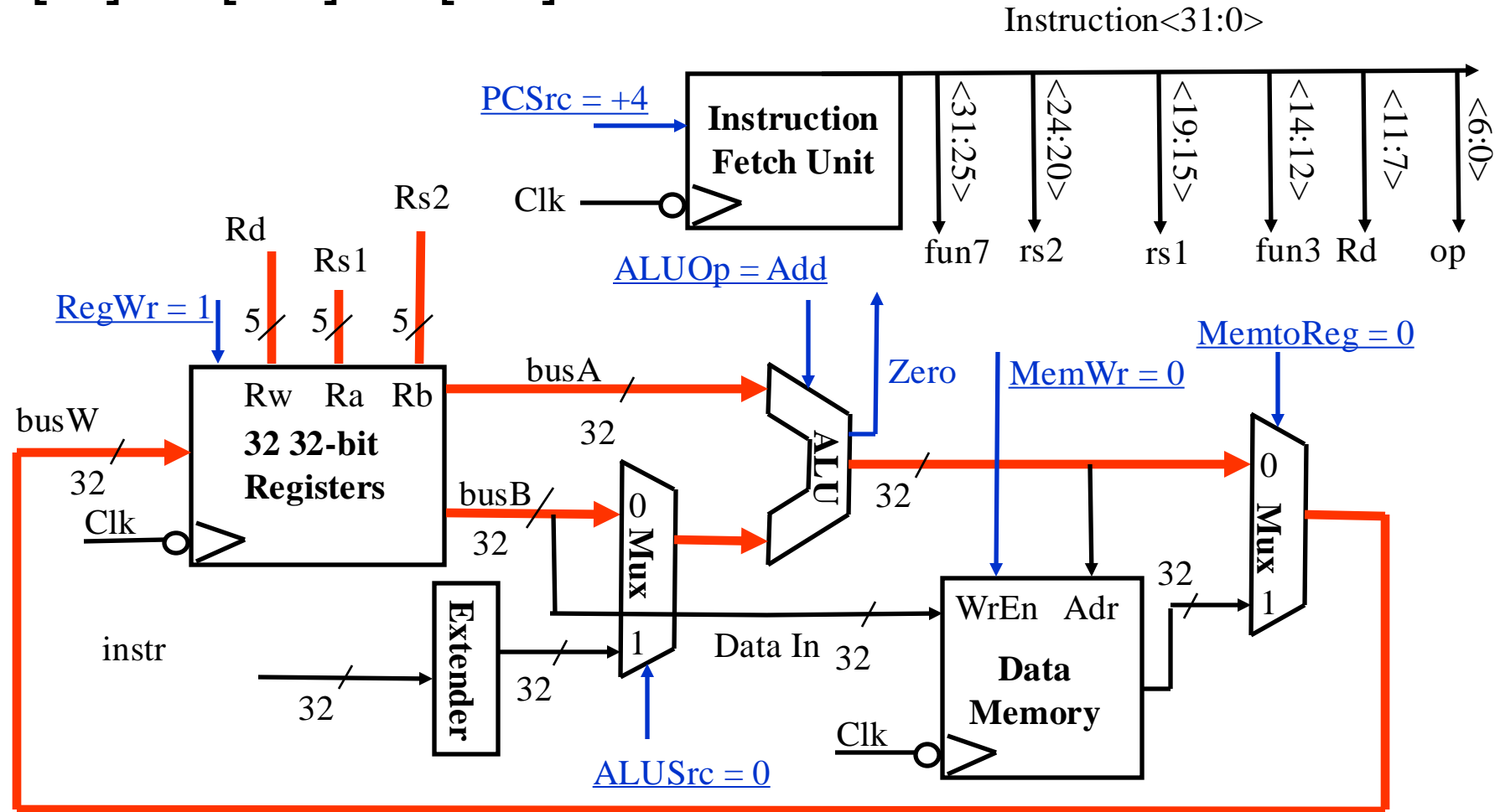

Meaning of Control Signals

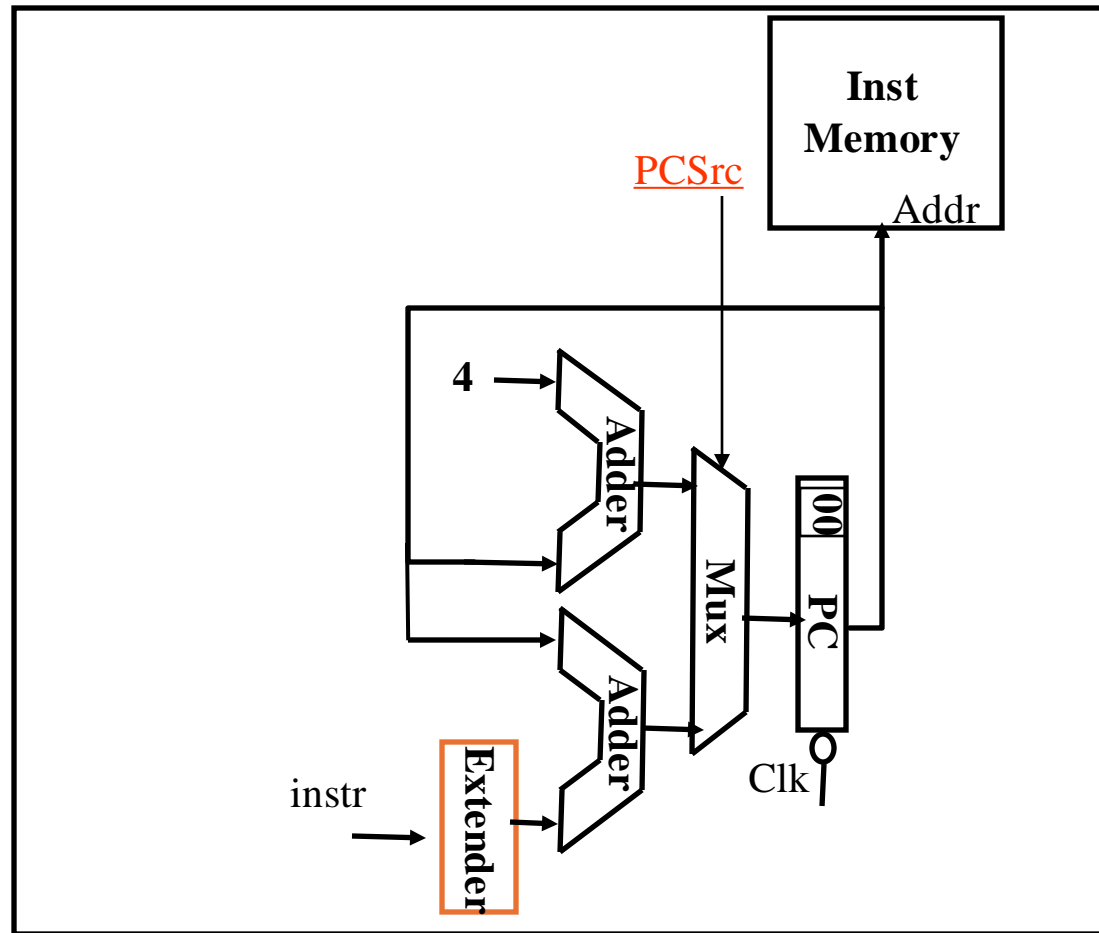
- rs1, rs2 and rd are hardwired in datapath
- PCSrc: 0 => $PC \leftarrow PC + 4$; 1 => $PC \leftarrow PC + \text{SignExt}(\text{imm12}) \parallel 0$



**Instruction
Fetch Unit**


Meaning of Control Signals

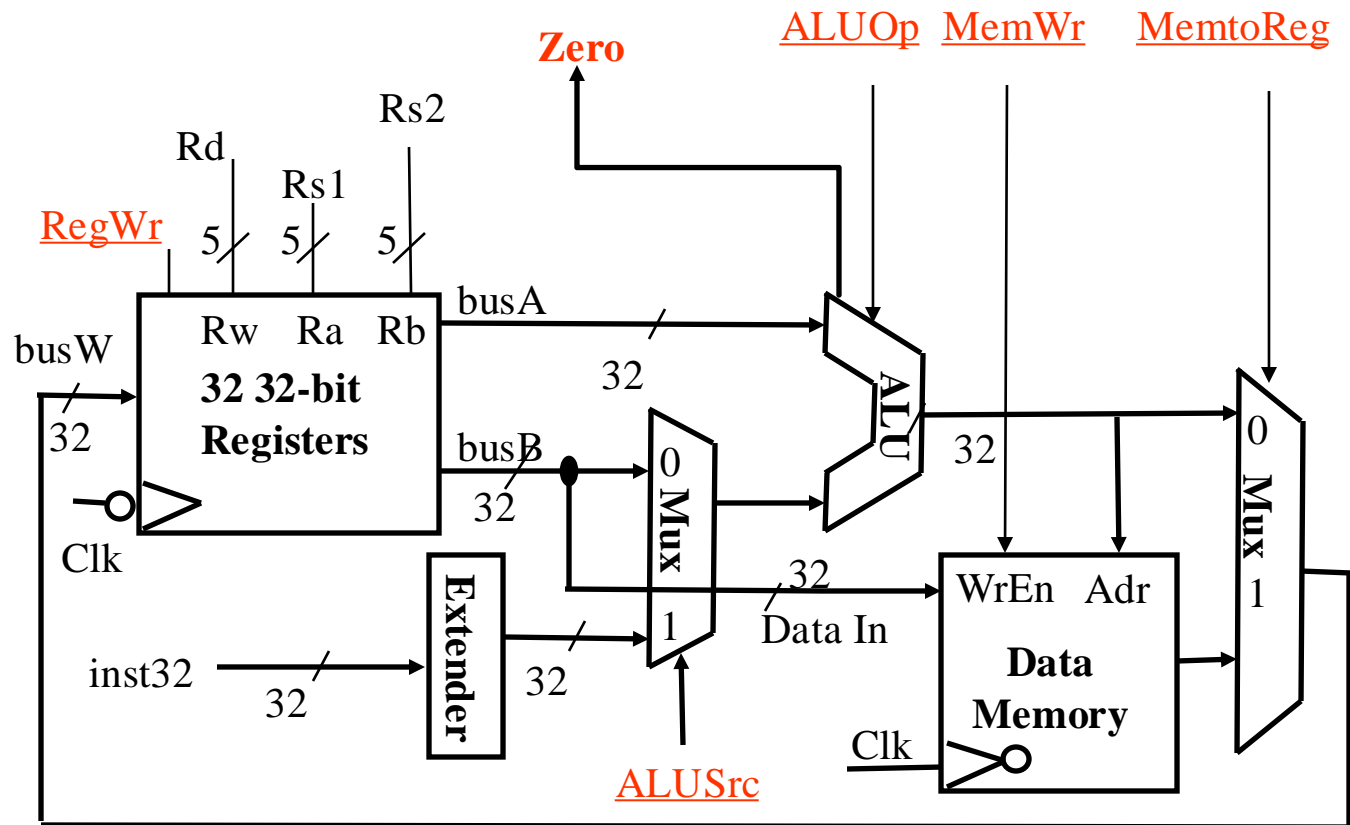- ALUSrc: 0 => regB; 1 => immed
- ALUOp: “add”, “sub”
- MemWr: write memory
- MemtoReg: 1=>Mem
- RegWr: write dest register




lw Controls

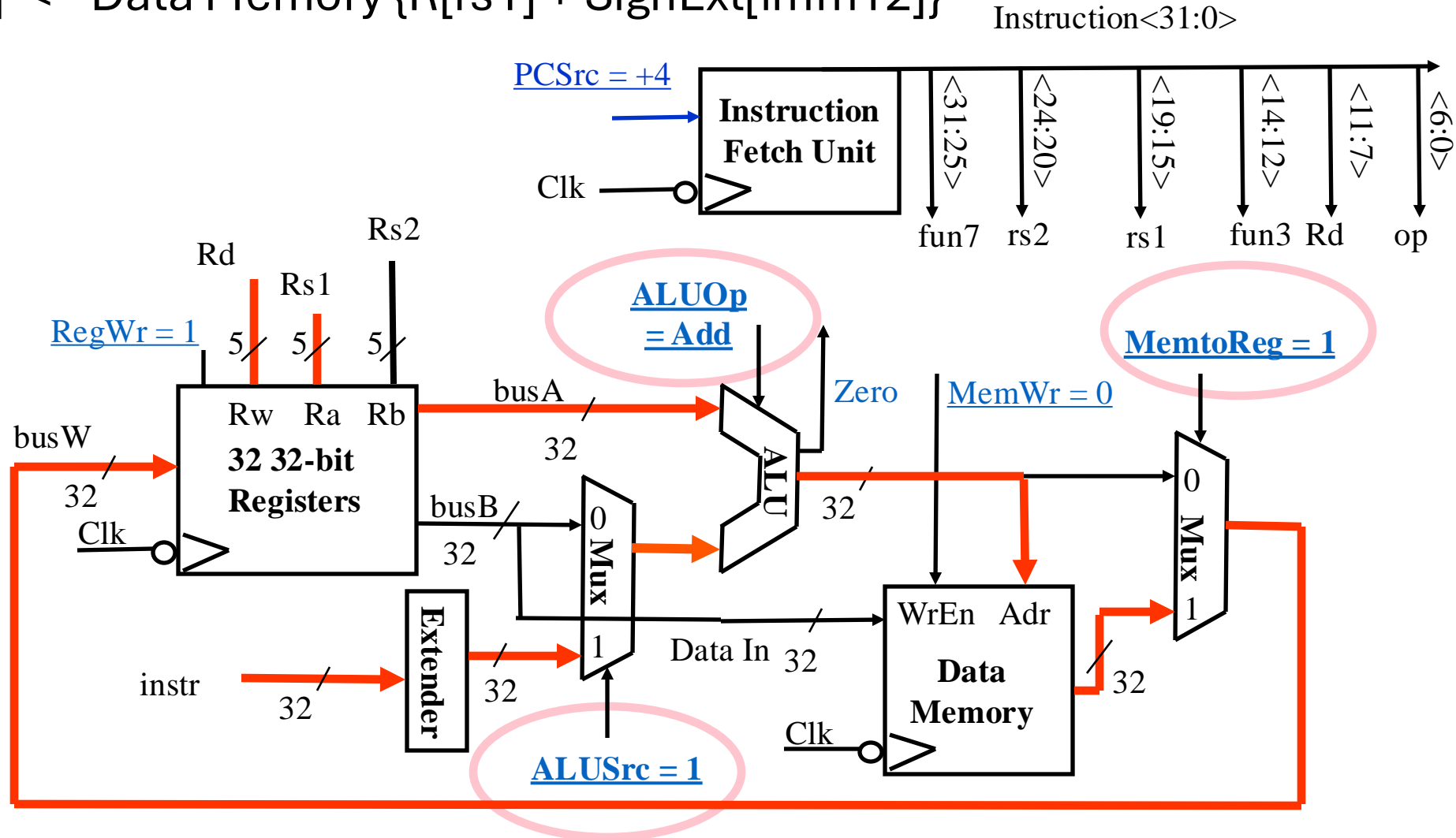- $R[rd] \leftarrow \text{Data Memory} \{R[rs1] + \text{SignExt}[imm12]\}$




sw Controls: Worksheet

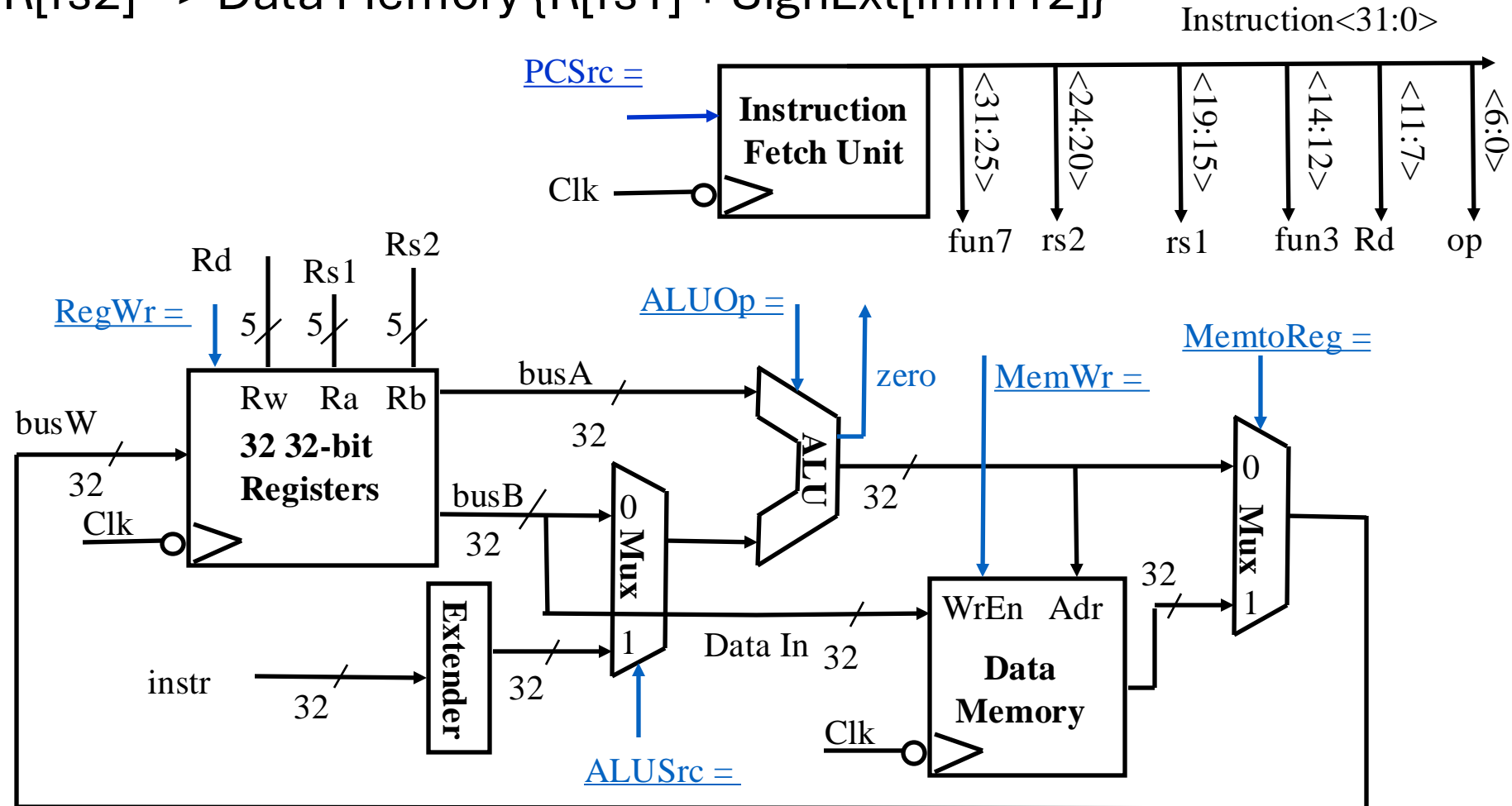- $R[rs2] \rightarrow \text{Data Memory } \{R[rs1] + \text{SignExt}[imm12]\}$




sw Controls: Solution

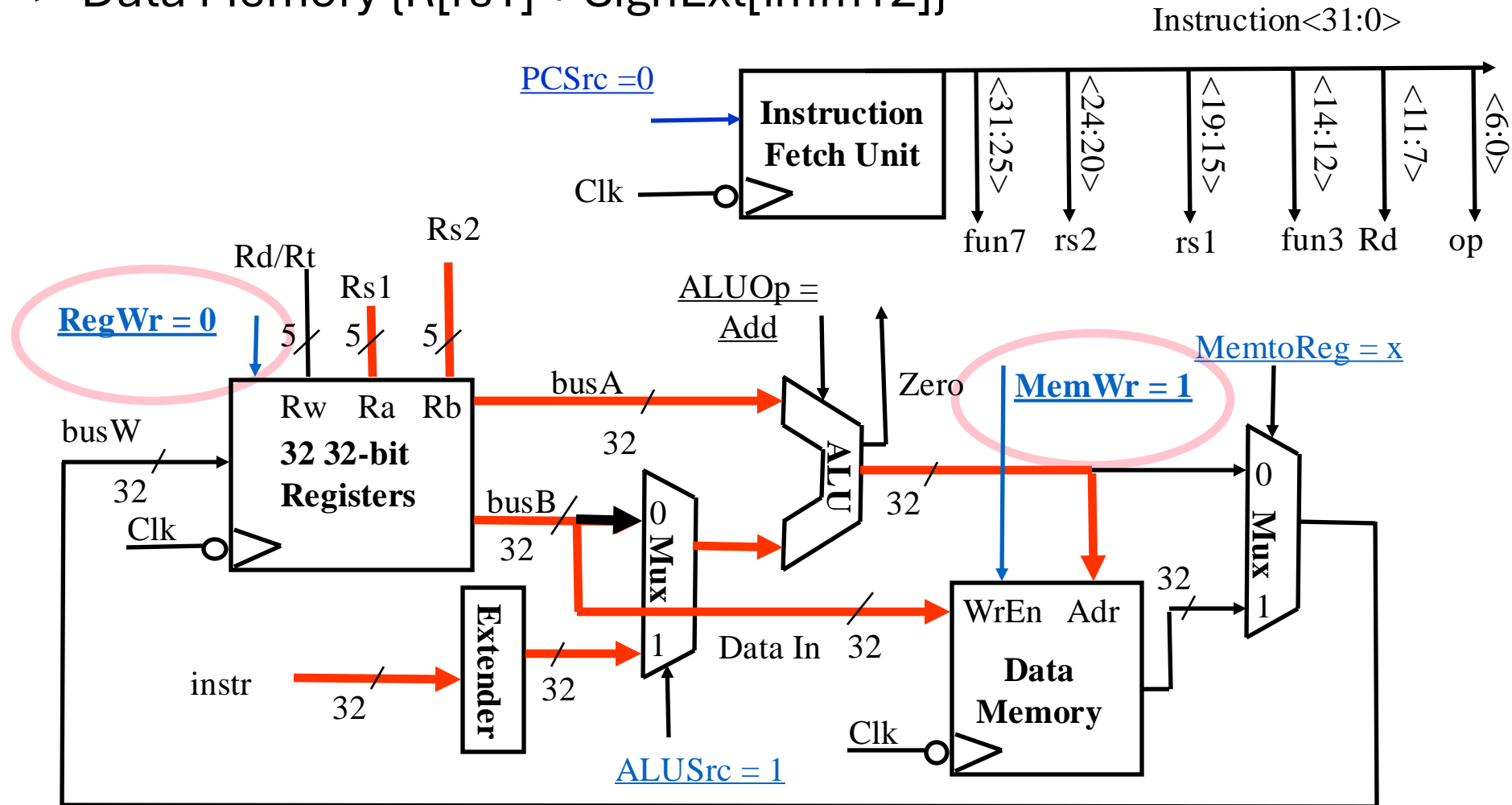- $R[rs2] \rightarrow \text{Data Memory} \{R[rs1] + \text{SignExt}[\text{imm12}]\}$



beq controls

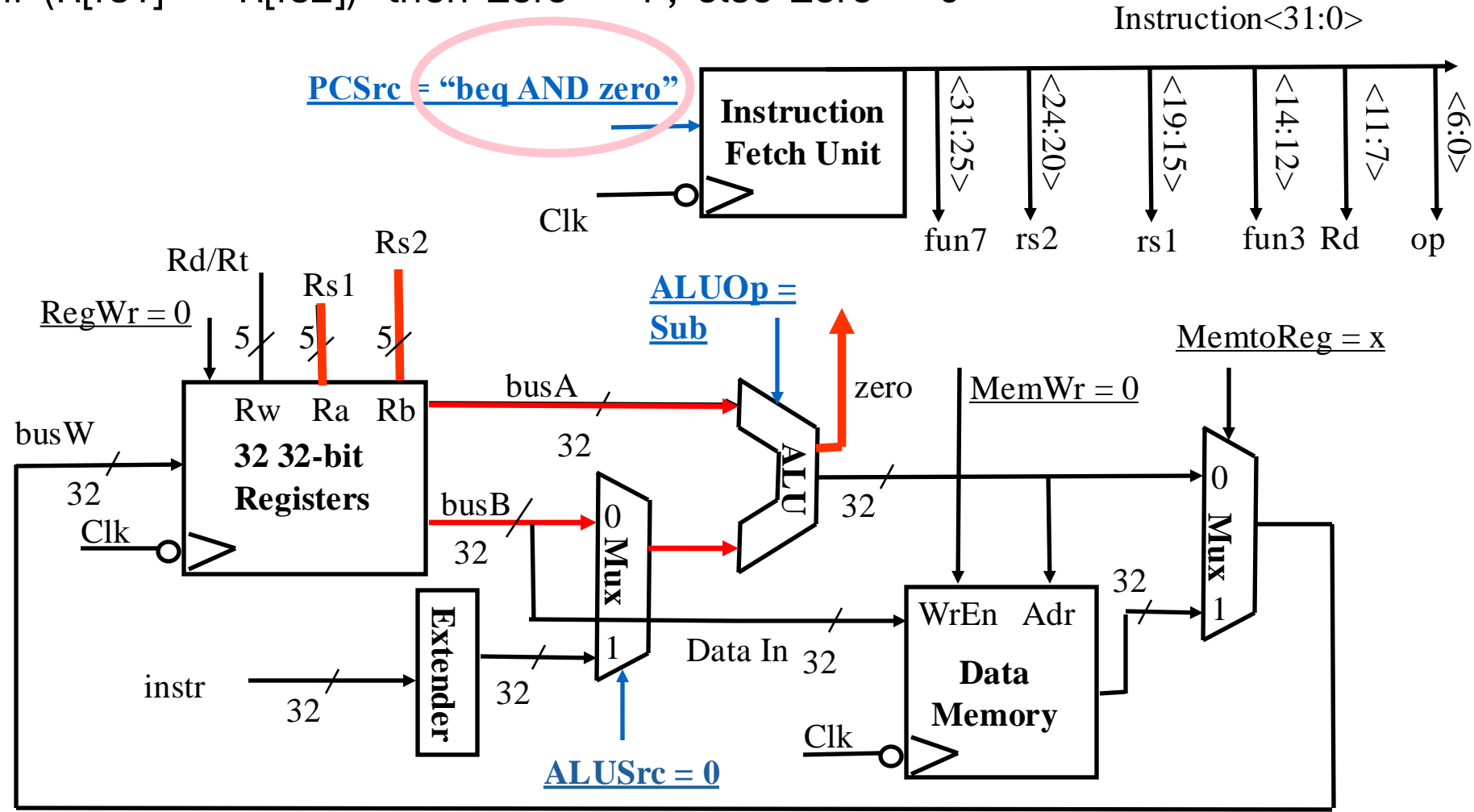- if ($R[rs1] == R[rs2]$) then Zero \leftarrow 1 ; else Zero \leftarrow 0



Summary of Control Signals

inst Register Transfer

ADD $R[rd] \leftarrow R[rs1] + R[rs2];$ $PC \leftarrow PC + 4$

$ALUsrc = \text{RegB}, ALUOp = \text{"add"}, \text{RegWr}, PCSrc = \text{"+4"}$

SUB $R[rd] \leftarrow R[rs1] - R[rs2];$ $PC \leftarrow PC + 4$

$ALUsrc = \text{RegB}, ALUOp = \text{"sub"}, \text{RegWr}, PCSrc = \text{"+4"}$

LOAD $R[rd] \leftarrow \text{MEM}[R[rs1] + \text{sign_ext}(\text{imm12})];$ $PC \leftarrow PC + 4$

$ALUsrc = \text{Im}, ALUOp = \text{"add"}, \text{MemtoReg}, \text{RegWr}, PCSrc = \text{"+4"}$

STORE $\text{MEM}[R[rs1] + \text{sign_ext}(\text{imm12})] \leftarrow R[rs2];$ $PC \leftarrow PC + 4$

$ALUsrc = \text{Im}, ALUOp = \text{"add"}, \text{MemWr}, PCSrc = \text{"+4"}$

BEQ $\text{if } (R[r1] == R[r2]) \text{ then } PC \leftarrow PC + \text{sign_ext}(\text{imm12}) || 0 \text{ else } PC \leftarrow PC + 4;$

$PCSrc = \text{"beq AND zero"}, ALUOp = \text{"sub"}$

Control Logic

- Logic must generate appropriate signals for all instructions
- Summary slide (previous)
 - A way of representing the truth table
- Till now: Instr \rightarrow signal, next: transpose
 - First: Equations in terms of opcodes
 - Next: Equations in terms of instruction bits


Controls: Logic equations

- PCSrc <= if (OP == BEQ) then "Zero" else 0
- ALUSrc <= if (OP == "R-type") then "regB"
elseif (OP == beq) then "regB"
else "imm"
- ALUOp <= if (OP == "R-type") then **funct**
elseif (OP == beq) then "sub"
else "add"
- MemWr <= _____
- MemtoReg <= _____
- RegWr: <= _____


Controls: Logic equations

- PCSrc <= if (OP == BEQ) then Zero else 0
- ALUsrc <= if (OP == "R-type") then "regB"
elseif (OP == BEQ) then regB, else "imm"
- ALUOp <= if (OP == "R-type") then **funct**
elseif (OP == BEQ) then "passThrough"
else "add"
- MemWr <= (OP == Store)
- MemtoReg <= (OP == Load)
- RegWr: <= if ((OP == Store) || (OP == BEQ)) then 0 else 1

Full Data Path with control

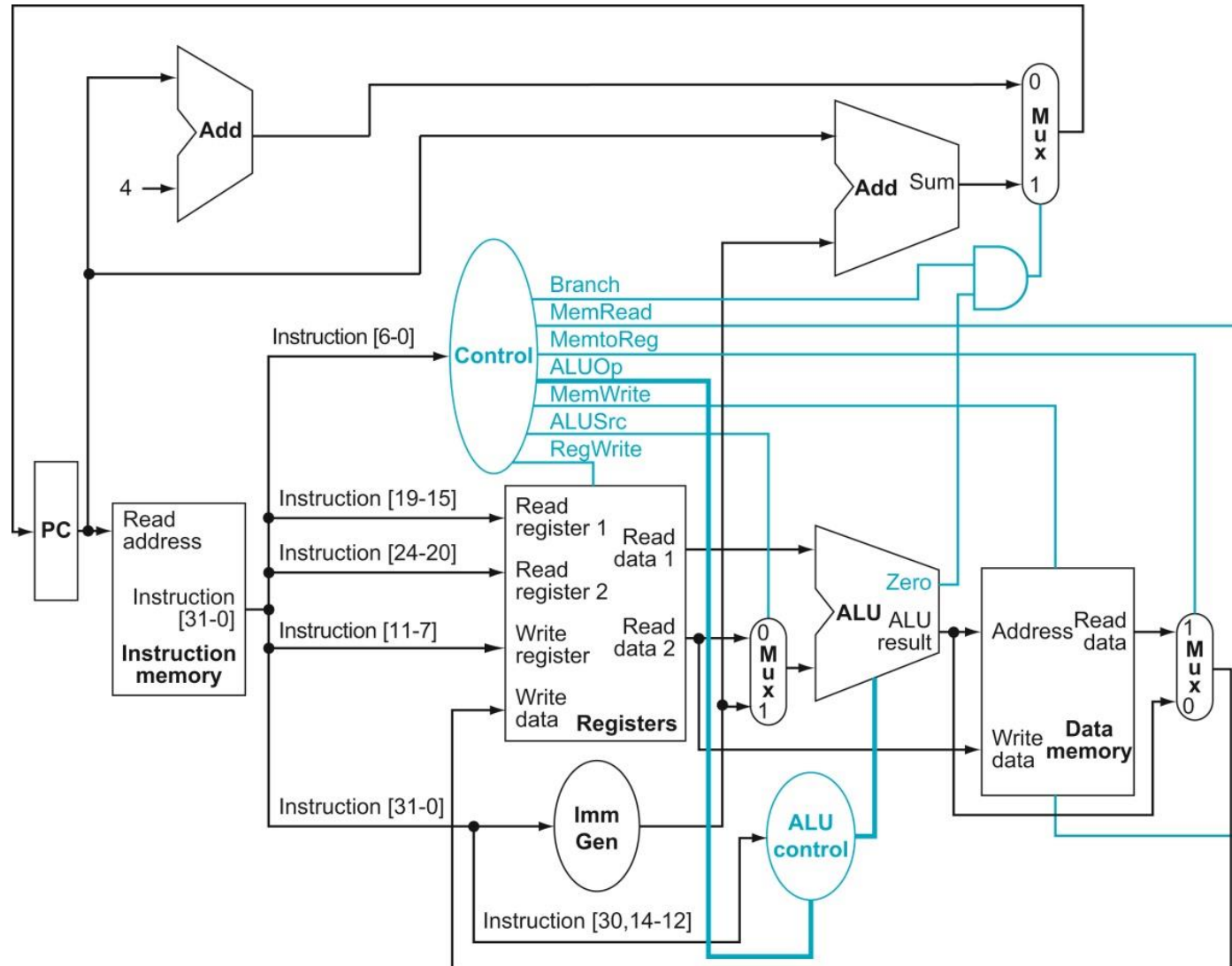

ALU Operations

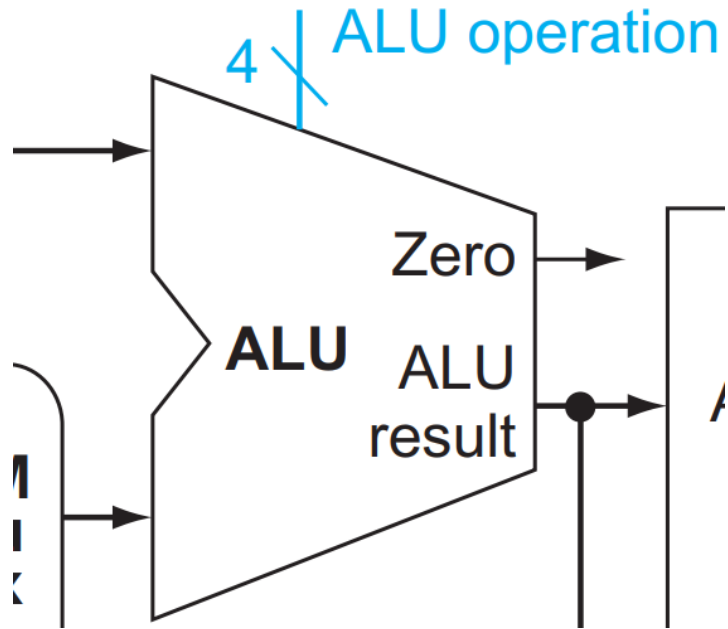

| ALU control lines | Function |
|-------------------|----------|
| 0000 | AND |
| 0001 | OR |
| 0010 | add |
| 0110 | subtract |

Concrete signals for the ALU


- We create a control signal called ALUOp
 - There are three different scenarios for ALU operation (lw/sw, beq, then R-type)
 - You only need to look at the func fields in R-Type

| Instruction opcode | ALUOp | Operation | Funct7 field | Funct3 field | Desired ALU action | ALU control input |
|--------------------|-------|-----------------|--------------|--------------|--------------------|-------------------|
| lw | 00 | load word | XXXXXXX | XXX | add | 0010 |
| sw | 00 | store word | XXXXXXX | XXX | add | 0010 |
| beq | 01 | branch if equal | XXXXXXX | XXX | subtract | 0110 |
| R-type | 10 | add | 0000000 | 000 | add | 0010 |
| R-type | 10 | sub | 0100000 | 000 | subtract | 0110 |
| R-type | 10 | and | 0000000 | 111 | AND | 0000 |
| R-type | 10 | or | 0000000 | 110 | OR | 0001 |

Multi-level control

- Based on a combination of the ALUOp and the func fields: set the ALU Operation

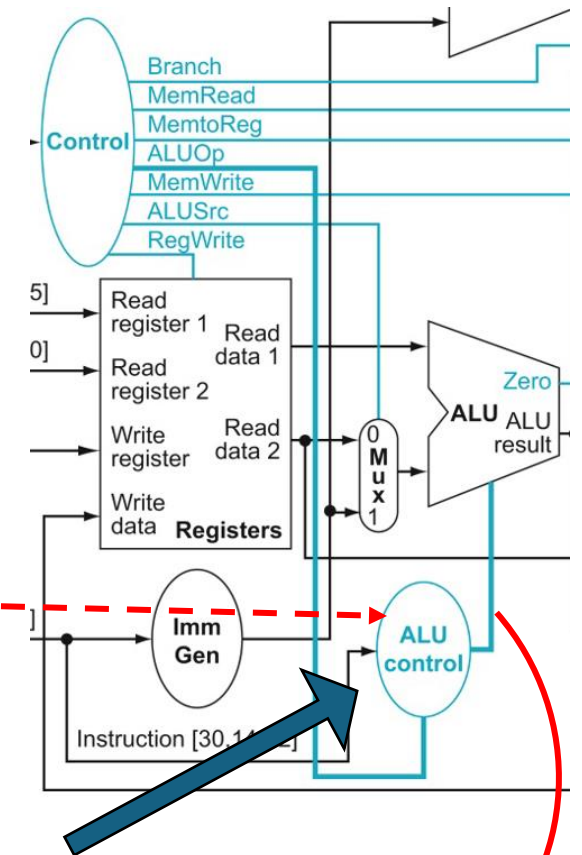Control contains combinational logic to set the signals





| | ALUOp | | Funct7 field | | | | | | | Funct3 field | | | Operation |
|--------|--------|--------|--------------|-------|-------|-------|-------|-------|-------|--------------|-------|-------|-----------|
| | ALUOp1 | ALUOp0 | I[31] | I[30] | I[29] | I[28] | I[27] | I[26] | I[25] | I[14] | I[13] | I[12] | |
| lw/sw | 0 | 0 | X | X | X | X | X | X | X | X | X | X | 0010 |
| beq | X | 1 | X | X | X | X | X | X | X | X | X | X | 0110 |
| R-type | 1 | X | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0010 |
| | 1 | X | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0110 |
| | 1 | X | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 0000 |
| | 1 | X | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 0 | 0001 |

| ALU control lines | Function |
|-------------------|----------|
| 0000 | AND |
| 0001 | OR |
| 0010 | add |
| 0110 | subtract |

Main Control Unit

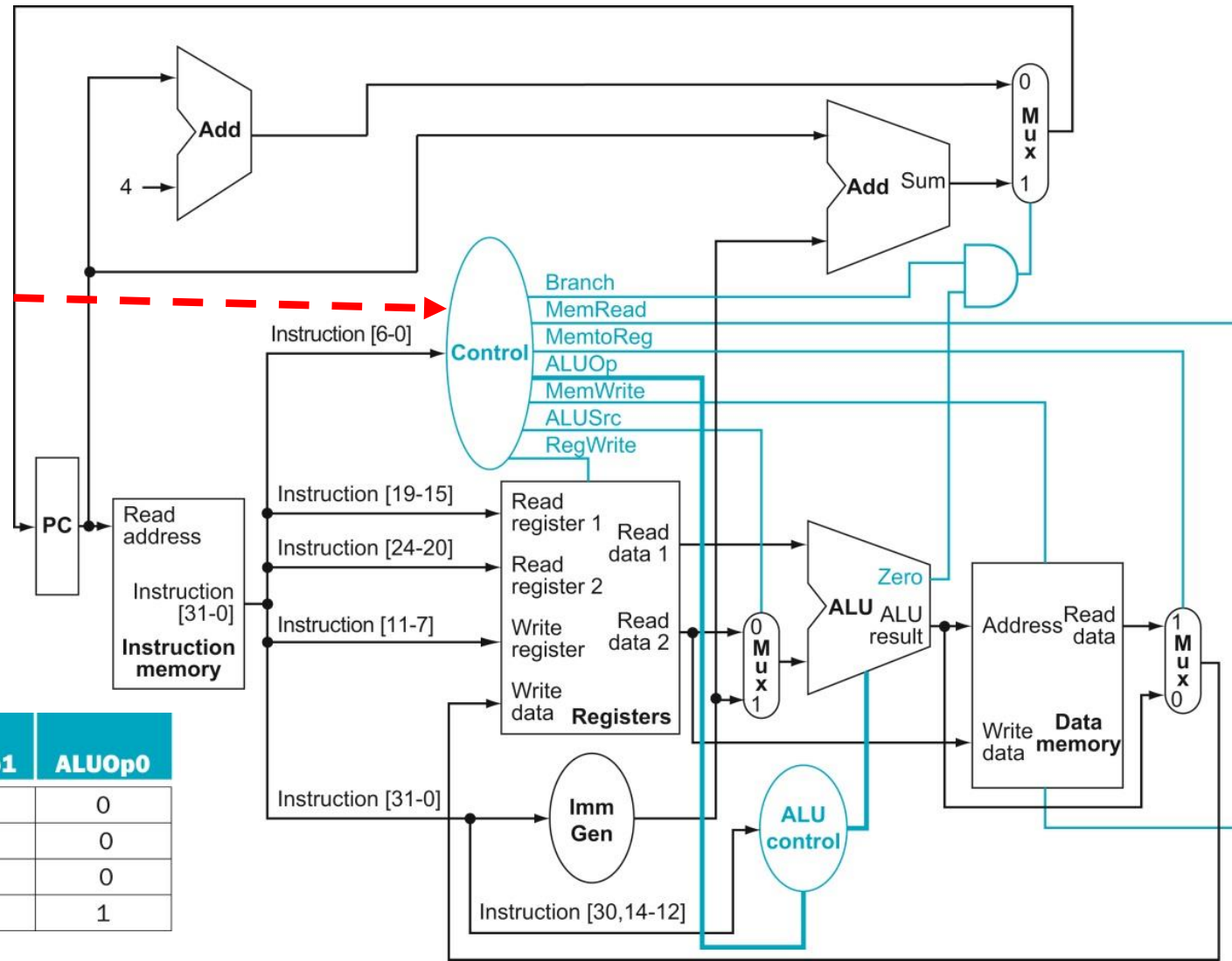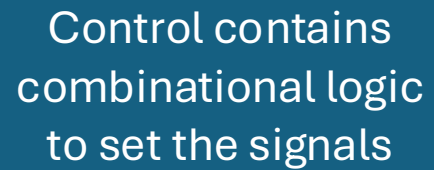
- Can determine these signals directly from the Op Code



| Instruction | ALUSrc | Memto-Reg | Reg-Write | Mem-Read | Mem-Write | Branch | ALUOp1 | ALUOp0 |
|-------------|--------|-----------|-----------|----------|-----------|--------|--------|--------|
| R-format | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 0 |
| lw | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 |
| sw | 1 | X | 0 | 0 | 1 | 0 | 0 | 0 |
| beq | 0 | X | 0 | 0 | 0 | 1 | 0 | 1 |

Immediate Generator

- Takes in the instruction, spits out a 32-bit immediate
- The table below maps the bits output by the unit to the instruction bits based on the instruction type
- **This table is without all the crazy bit-swizzling**

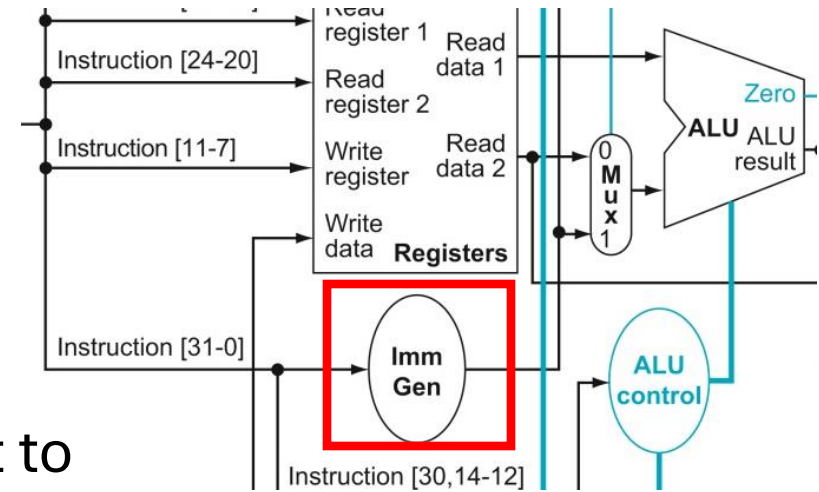[illegible]

The more inputs you have to select each bit, the wider the internal mux needed to implement the bit

Immediate Generator

Now, let's
add the
swizzling!

| Name (Field size) | Field | | | | | | Comments |
|----------------------|-----------------------------|--------|--------|--------|---------------|--------|-------------------------------|
| | 7 bits | 5 bits | 5 bits | 3 bits | 5 bits | 7 bits | |
| R-type | funct7 | rs2 | rs1 | funct3 | rd | opcode | Arithmetic instruction format |
| I-type | immediate[11:0] | | rs1 | funct3 | rd | opcode | Loads & immediate arithmetic |
| S-type | immed[11:5] | rs2 | rs1 | funct3 | immed[4:0] | opcode | Stores |
| SB-type | immed[12,10:5] | rs2 | rs1 | funct3 | immed[4:1,11] | opcode | Conditional branch format |
| UJ-type | immediate[20,10:1,11,19:12] | | | | rd | opcode | Unconditional jump format |
| U-type | immediate[31:12] | | | | rd | opcode | Upper immediate format |

No Swizzle

[illegible]


With Swizzle

| | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
|-------------------|--------|-----------------------------|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|----|
| | | Immediate Output Bit by Bit | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| | | 31 | 30 | 29 | 28 | 27 | 26 | 25 | 24 | 23 | 22 | 21 | 20 | 19 | 18 | 17 | 16 | 15 | 14 | 13 | 12 | 11 | 10 | 9 | 8 | 7 | 6 | 5 | 4 | 3 | 2 | 1 | 0 |
| Instruction | Format | Immediate Input Bit by Bit | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| Load, Arith. Imm. | I | i31 | i31 | i31 | i31 | i31 | i31 | i31 | i31 | i31 | i31 | i31 | i31 | i31 | i31 | i31 | i31 | i31 | i31 | i31 | i31 | i30 | i29 | i28 | i27 | i26 | i25 | i24 | i23 | i22 | i21 | i20 | |
| Store | S | " | " | " | " | " | " | " | " | " | " | " | " | " | " | " | " | " | " | " | " | " | " | " | " | " | " | " | i11 | i10 | i9 | i8 | i7 |
| Cond. Branch | SB | " | " | " | " | " | " | " | " | " | " | " | " | " | " | " | " | " | " | " | " | i7 | " | " | " | " | " | " | " | " | " | " | 0 |
| Uncond. Jump | UJ | " | " | " | " | " | " | " | " | " | " | " | " | i19 | i18 | i17 | i16 | i15 | i14 | i13 | i12 | i20 | " | " | " | " | " | " | " | " | " | " | " |
| Load Upper Imm. | U | " | i30 | i29 | i28 | i27 | i26 | i25 | i24 | i23 | i22 | i21 | i20 | " | " | " | " | " | " | " | " | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | " |
| Unique Inputs | | 1 | 2 | 2 | 2 | 2 | 2 | 2 | 2 | 2 | 2 | 2 | 2 | 2 | 2 | 2 | 2 | 2 | 2 | 2 | 2 | 4 | 2 | 2 | 2 | 2 | 2 | 2 | 3 | 3 | 3 | 3 | 3 |


Why Swizzling

- Allows for simpler hardware
 - This small optimization doesn't matter in a big, complex implementation of RISC-V.
 - Saves area, energy, and latency in a simple implementation where every gate matters.
- It makes the assembler's life a little more complicated
 - But it is not too bad – program knows the pattern, repeats
 - **Does, however, make the binary encoding harder to read**
 - **And makes it harder to encode/decode by hand :)**

Now you've seen all of it!

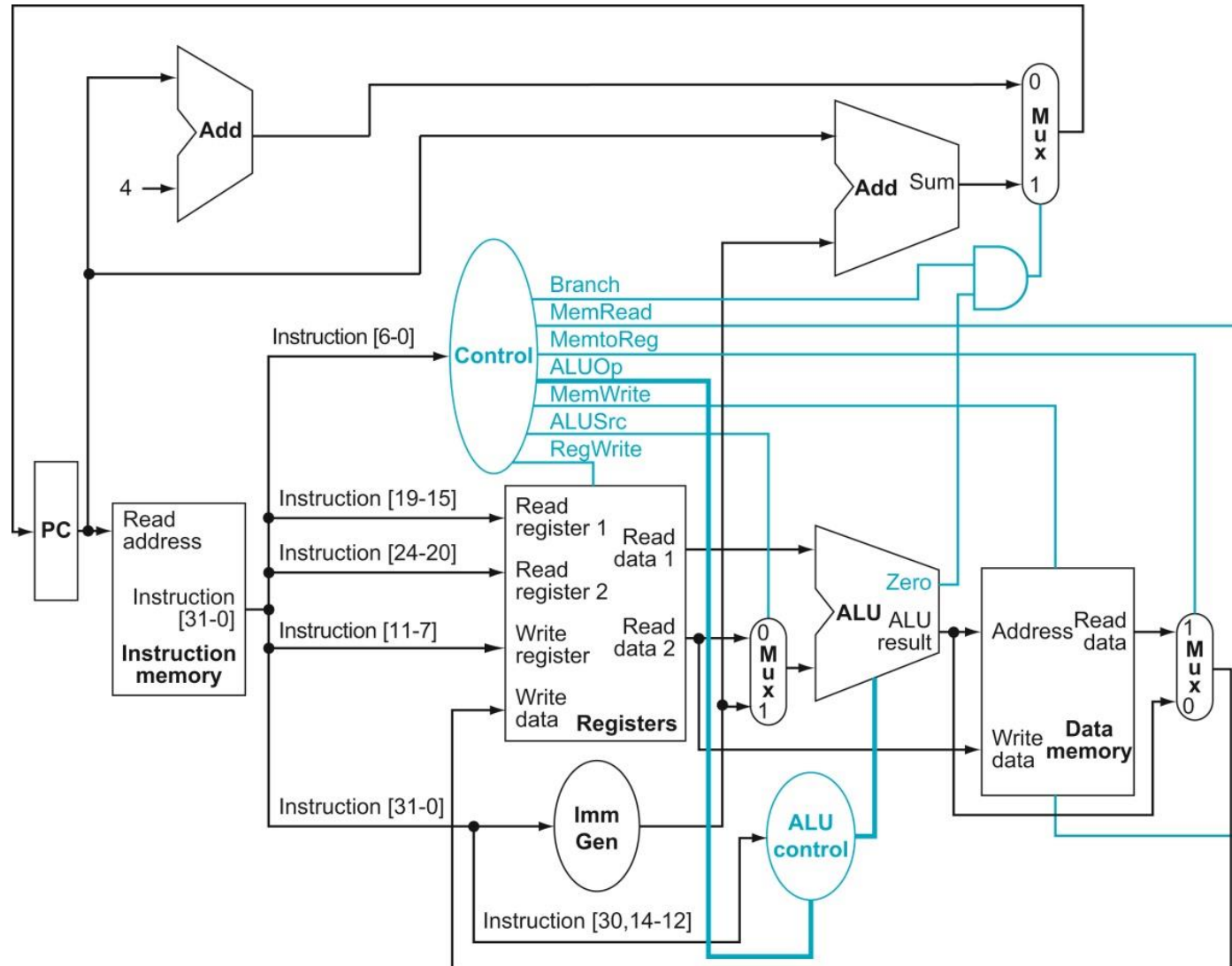


Cycletime

 

- What should the clock period be?
 - Enough to compute the next state values
 - Propagation clk-to-Q (new state)
 - Comb. Logic delay
 - Setup requirements

“lw” Instruction

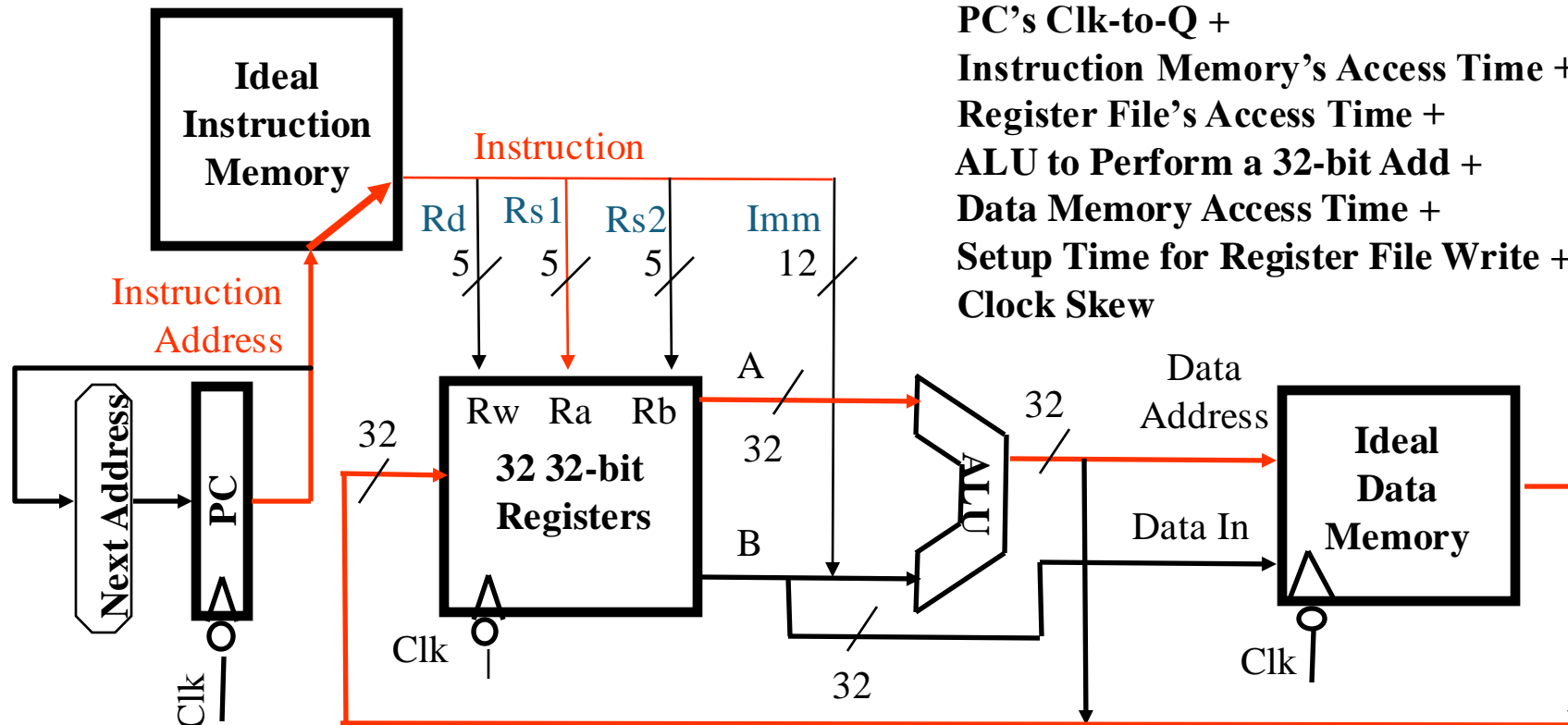
- Longer critical path
 - lower bound on cycletime



Critical Path (Load Operation) =
PC's Clk-to-Q +
Instruction Memory's Access Time +
Register File's Access Time +
ALU to Perform a 32-bit Add +
Data Memory Access Time +
Setup Time for Register File Write +
Clock Skew

What's wrong with our processor?

Arithmetic & Logical

 

Load



Store



Branch



- LOOOOONG Cycle Time
- ALL instructions take as much time as the slowest
- Real memory MUCH slower than our idealized memory
 - Today some 100ns (memory+bus+control) vs. 0.25ns CPU clock
 - cannot finish in one (short) cycle

Again, take 437!